

CSCE 312: Computer Organization

David Kebo HOUNGNINOU

Digital Logic Design

Sequential Systems

Combinational logic circuits:

Output values only depend on present **input values**.

Sequential logic circuits:


Output values depend on **input values** and the **state**.

Sequential circuits must have a way to retain **states** with memory devices.

Sequential logic circuits can be **synchronous** or **asynchronous**:

- A synchronous sequential circuit uses a clock signal to control the changes between states.
- An asynchronous sequential circuit does not use a clock.

Sequential System Diagram

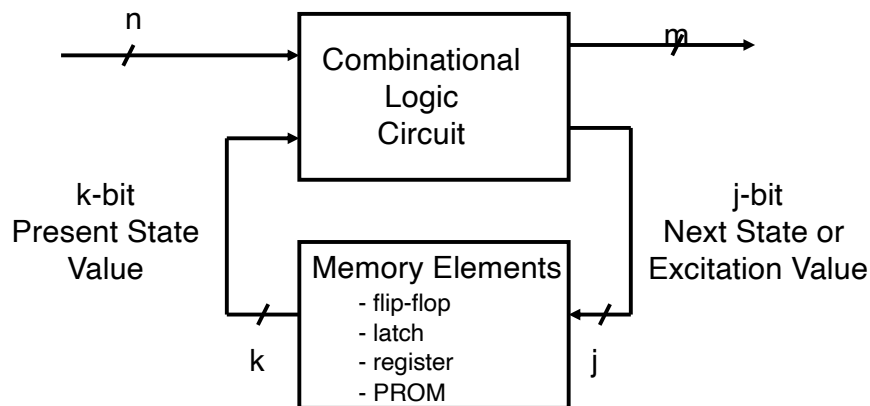

Mealy finite state machine


The m outputs depend on k present state bits and n inputs.

Moore finite state machine


The m outputs only depend on k present state bits

Remember: *Moore is Less!*

Controller Block Diagrams

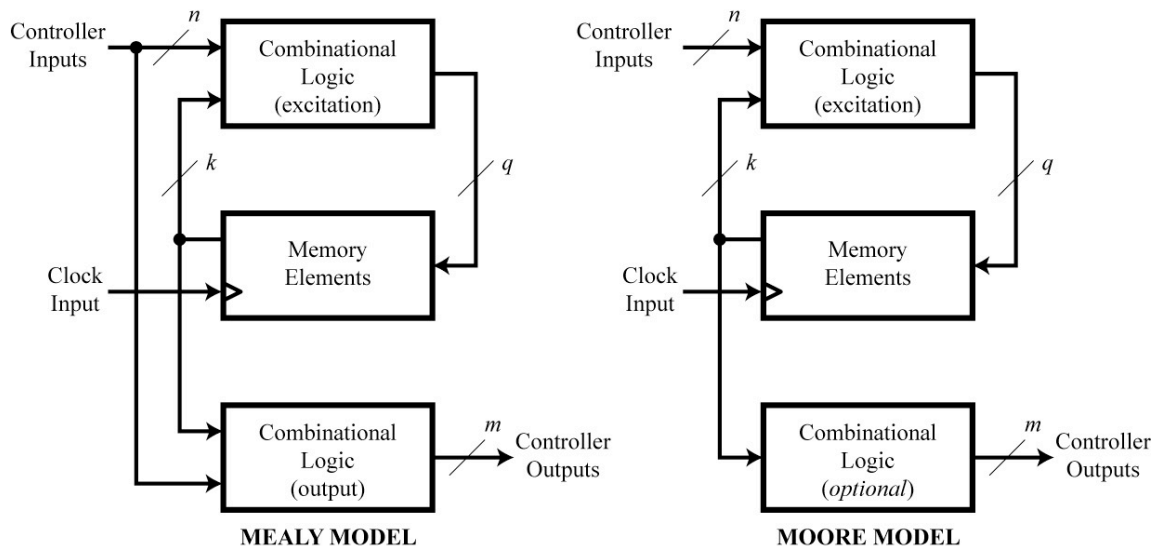

Clock Signal

 

τ : period (in seconds)

f : frequency (in Hertz) = $1/\tau$

duty cycle: ratio of pulse width to period (%)


$D_c = P_w / \tau$

P_w : pulse width (in seconds)

millisecond (ms) 10^{-3}	Kilohertz (kHz) 10^3
microsecond (μ s) 10^{-6}	Megahertz (MHz) 10^6
nanosecond (ns) 10^{-9}	Gigahertz (GHz) 10^9

Microprocessor clock frequency

AMD Ryzen™ 9 3900X

 Graphics Model: Discrete Graphics Card Required
of CPU Cores: 12
of Threads: 24
Max Boost Clock  Up to 4.6GHz
Base Clock: 3.8GHz



Intel® Core™ i9-9900K Processor

16M Cache, up to 5.00 GHz

A microprocessor frequency is the internal frequency of CPU core.

The higher the frequency, the faster the processor is!

Another factor of performance is the number of Instructions Per Clock that the CPU can process (IPC).

The clock frequency and the IPC give us the total number of instructions per second that the CPU can process:

$$\# \text{ of instructions/second} = \text{Frequency} * \text{IPC}$$

Clock Signal Example

What is the pulse-width of a 4.77 MHz clock with a 30% duty cycle?

Clock Signal Example

What is the pulse-width of a 4.77 MHz clock with a 30% duty cycle?

$$\tau = 1/f = (4.77 \times 10^6)^{-1} = 2.096 \times 10^{-7} = 210 \text{ ns}$$

Clock Signal Example

What is the pulse-width of a 4.77 MHz clock with a 30% duty cycle?

$$\tau = 1/f = (4.77 \times 10^6)^{-1} = 2.096 \times 10^{-7} = 210 \text{ ns}$$


$$P_w = (\text{duty cycle}) \times \tau = (0.3) \times (210 \text{ ns}) = 63 \text{ ns}$$

Storage Elements

 
(a) level-sensitive storage element (D-latch)

```

always @(g or d)
begin
    if (g) q <= d;
end
    
```



latch is transparent to changes on d

 


q follows d when g is high

 
(b) edge-triggered storage element (data flip-flop, or DFF)

```

always @(posedge clk)
begin
    q <= d;
end
    
```




capture the d input

 


q follows d on rising edge of clk


D-Latch operation

 


DFF operation

 

DFF operation

 

D FF, D-Latch operation

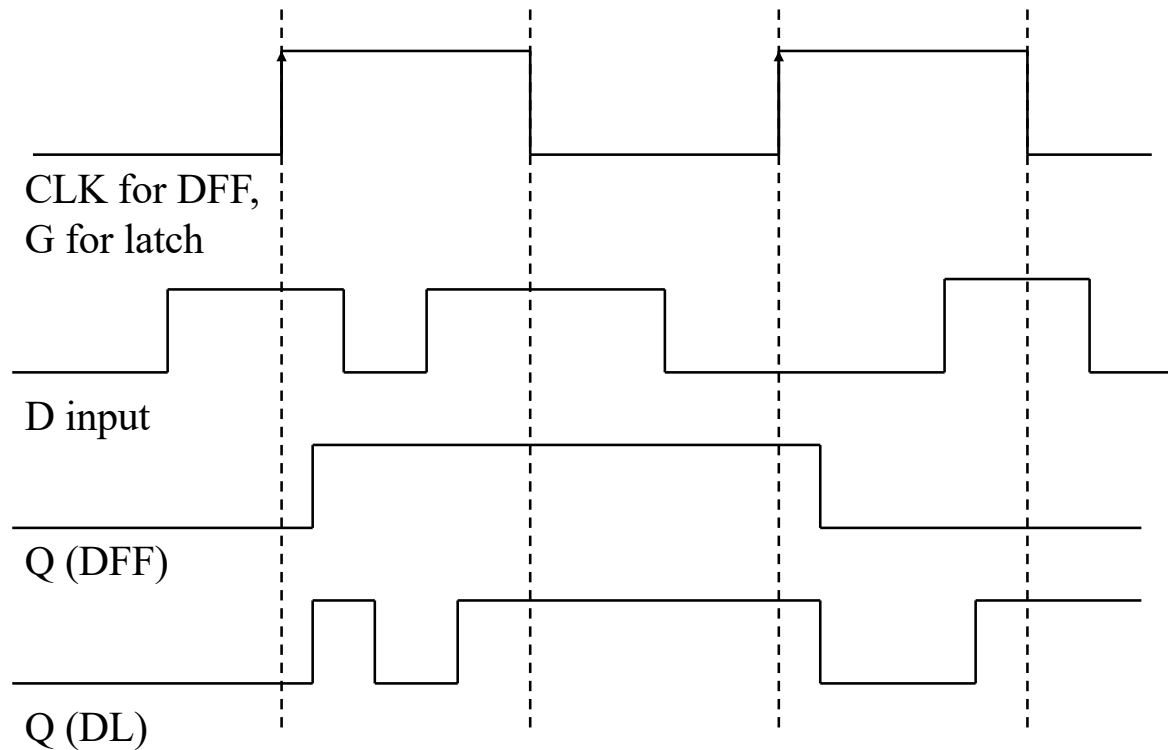


Houngninou

CSCE 312: Computer Organization

15


Other State Elements

 

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

JK can be useful for
single bit flags with
separate set(J),
reset(K) control.

RARELY USED

 

T	Q(t+1)
0	Q(t)
1	Q'(t)

Can be useful for
asynchronous counter
design.

RARELY USED

Houngninou

CSCE 312: Computer Organization


16

Synchronous vs Asynchronous inputs


Synchronous input: Output changes after active clock edge

Asynchronous input: Output changes independently of clock

 - State elements often have an asynchronous set and reset control.
- The D input is synchronous with respect to Clk.
- S and R are **asynchronous** inputs. S and R can change the output Q independently of Clk.
- Asynchronous inputs are dominant over Clk.




D FF with async control

 

D-Flip-Flop with Async. Set/Res


(a) DFF with asynchronous Set/Reset

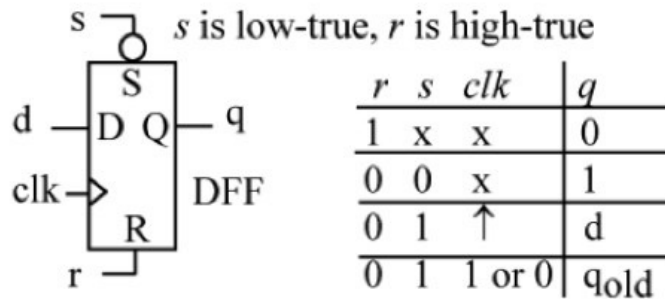

```
always @ (posedge clk or
          posedge r or
          negedge s)
```

```
begin
    if (r) q <= 1'b0;
    else if (!s) q <= 1'b0;
    else q <= d;
end
```


D-Flip-Flop with Async. Set/Res

 

1. d input is captured on rising clock edge as r, s are negated; q becomes '1'.
2. r input is asserted; q becomes '0'.
3. s input is asserted; q becomes '1'.
4. assertion of s input (a) overrides clock input (b), so q output remains as '1'.


D-Flip-Flop with Sync. Set/Res

(b) DFF with synchronous preset/clear

 

```
always @(posedge clk)
begin
    q <= d; //lowest priority
    if (!pre) q <= 1'b1;
    if (clr) q <= 0'b0; //highest priority
end
```

D-Flip-Flop with Sync. Set/Res

 

1. *d* input is captured on rising clock edge as *clr*, *pre* are negated; *q* becomes '1'.
2. assertion of synchronous input has no effect if does not occur on the active clock edge
3. *clr* input is asserted on rising clock edge; *q* becomes '0'.
4. *pre* input is asserted on rising clock edge; *q* becomes '1'.

FF Timing: Propagation Delay

- **C2Q**: Q will change some propagation delay after change in C. Value of Q is based on D input for DFF.
- **S2Q, R2Q**: Q will change some propagation delay after change on S input, R input
- Note that there is NO propagation delay D2Q for DFF!
- D is a Synchronous INPUT, no prop delay value for synchronous inputs


Setup, Hold Times

Synchronous inputs (e.g. D) have Setup, Hold time specification with respect to the CLOCK input

Setup Time: the amount of time the synchronous input (D) must be stable **before** the active edge of clock.

Hold Time: the amount of time the synchronous input (D) must be stable **after** the active edge of clock.

Setup, Hold Time

 


If changes on D input violate either setup or hold time, then correct FF operation is not guaranteed.

Setup/Hold measured around active clock edge.

Registers

The most common sequential building block is the register.

 A register is n bits wide, and has a load line for loading in a new value into the register.




Register contents do not change unless $LD = 1$ on active edge of clock.

A DFF is NOT a register!

DFF contents change every clock edge.

$ACLR$ used to asynchronously clear the register


1 Bit Register using DFF, Mux

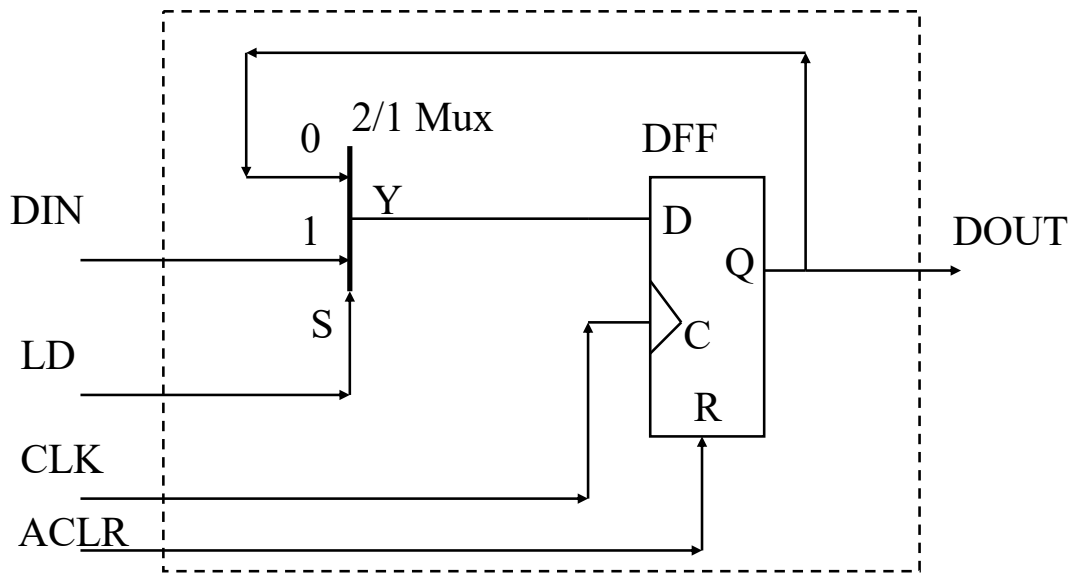

Note that the DFF simply loads an old value when LD = 0.

DFF is loaded every clock cycle.



1 Bit Register using Gated Clock

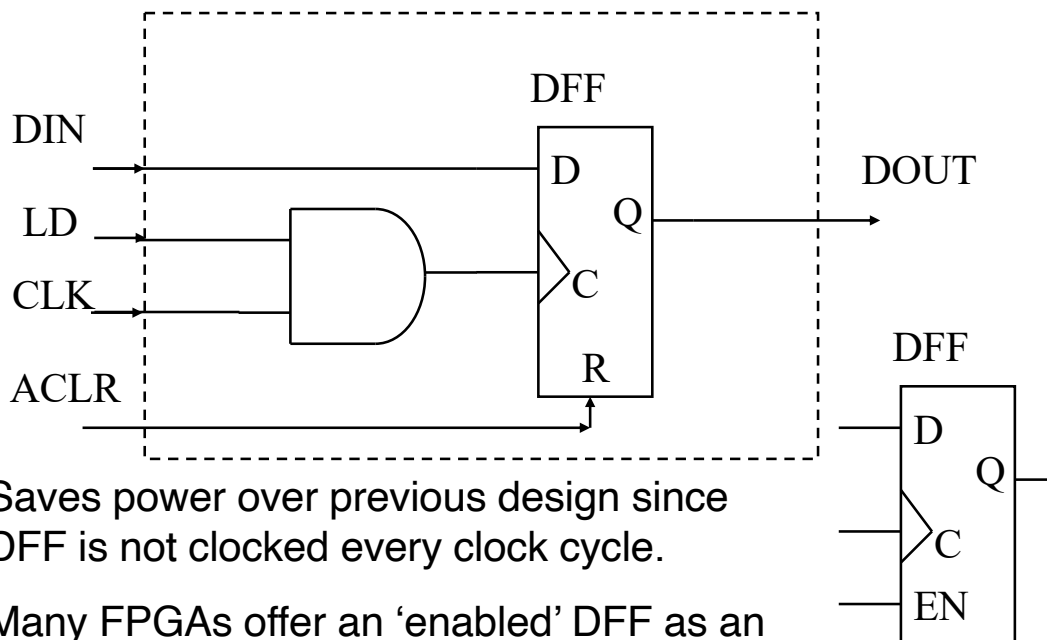

Saves power over previous design since DFF is not clocked every clock cycle.

Many FPGAs offer an 'enabled' DFF as an integrated unit.

8-bit Register

  

```

module reg8bit(clk,r,d,ld,q);
    input clk,r,ld;
    input [7:0] d;
    output [7:0] q;


    reg [7:0] q;

    //register
    always @(posedge clk
              or negedge r)
    begin
        //async reset
        if (!r) q <= 8'b0;
        else begin
            //synchronous inputs
            if (ld) q <= d;
        end
    end
endmodule

```

Counter

 Very useful sequential building block. Used to generate memory addresses, or keep track of the number of times a datapath operation is performed.




LD asserted: loads counter with DIN value.

CNT_EN asserted will increment counter on next active clock edge.

ACLR will asynchronously clear the counter.

One way to build a Counter

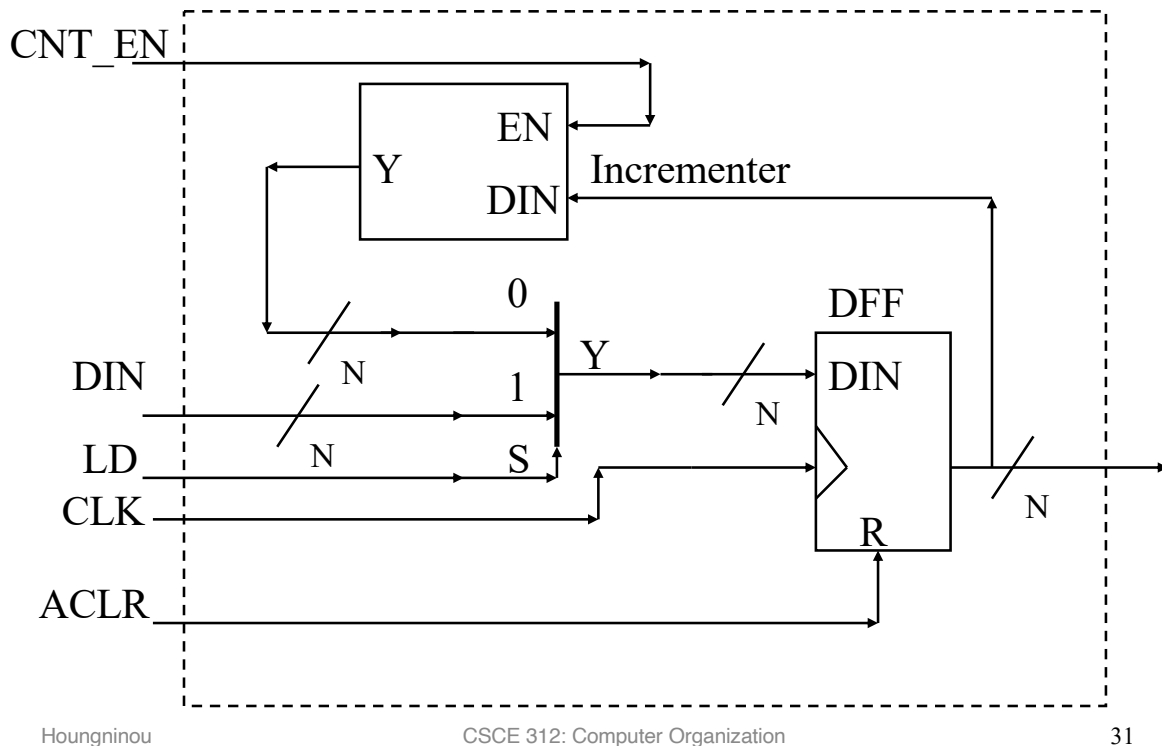


Houngninou

CSCE 312: Computer Organization


31

 Incrementer: Combinational Building Block



When $EN=1$, $Y = DIN + 1$

When $EN=0$, $Y = DIN$

 


Houngninou

CSCE 312: Computer Organization

32


8-bit Counter

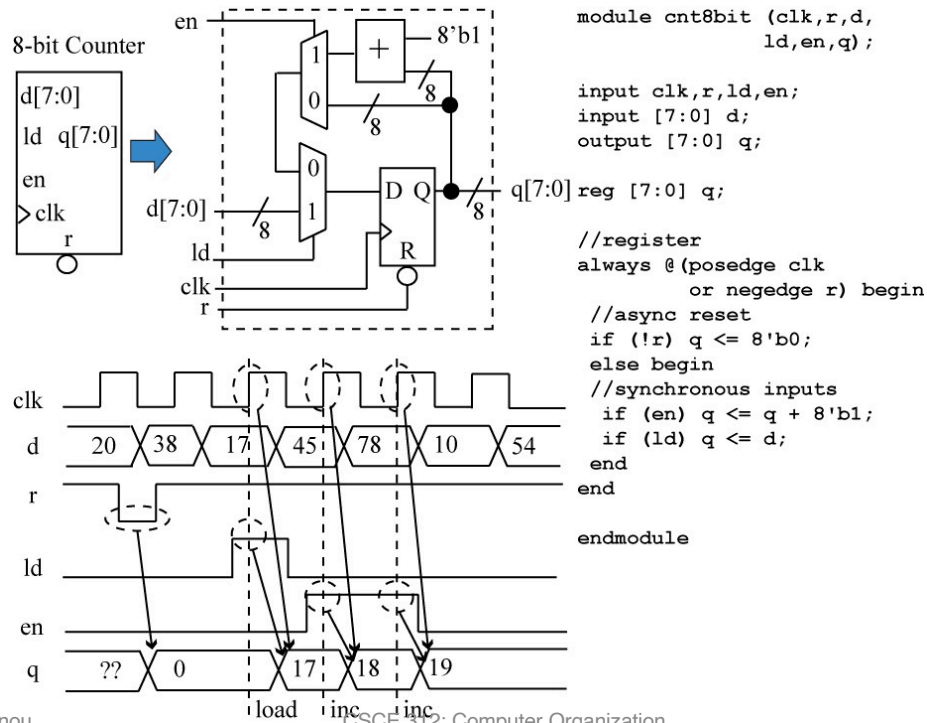


Describing FSMs

1. State Tables
2. State Equations
3. State Diagrams
4. Algorithmic State Machine (ASM) Charts
 1. Preferred method in this class
5. HDL descriptions

Example State Machine

 

State Diagram
(Bubble Diagram)

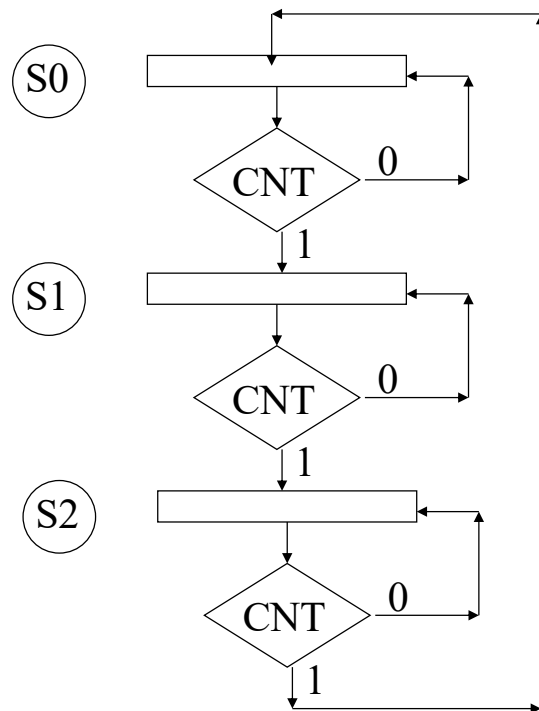


ASM Chart

ASM Chart Symbols




State-Representing
Symbol

 

Basic Decision
Symbol



Conditional Output
Symbol

 

Flow Direction
Symbol

FSM Implementation

Use DFFs, State assignment: S0 = 00, S1 = 01, S2 = 10

PS			NS			
CNT	Q1	Q0	Q1	Q0	D1	D0
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	0	1	0
0	1	1	x	x	x	x
1	0	0	0	1	0	1
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	1	x	x	x	x

State Table

Equations

$$D1 = \text{CNT}'Q1Q0' + \text{CNT} Q1'Q0$$

$$D0 = \text{CNT}'Q1'Q0 + \text{CNT} Q1'Q0'$$

Minimize Equations

D1

		Q1Q0			
		00	01	11	10
CNT	0	0	0	x	1
	1	0	1	x	0


$$D1 = \text{CNT}'Q1 + \text{CNT} Q0$$

D0


		Q1Q0			
		00	01	11	10
CNT	0	0	1	x	0
	1	1	0	x	0

$$D0 = \text{CNT}'Q0 + \text{CNT} Q1'Q0'$$

FSMD Block Diagram

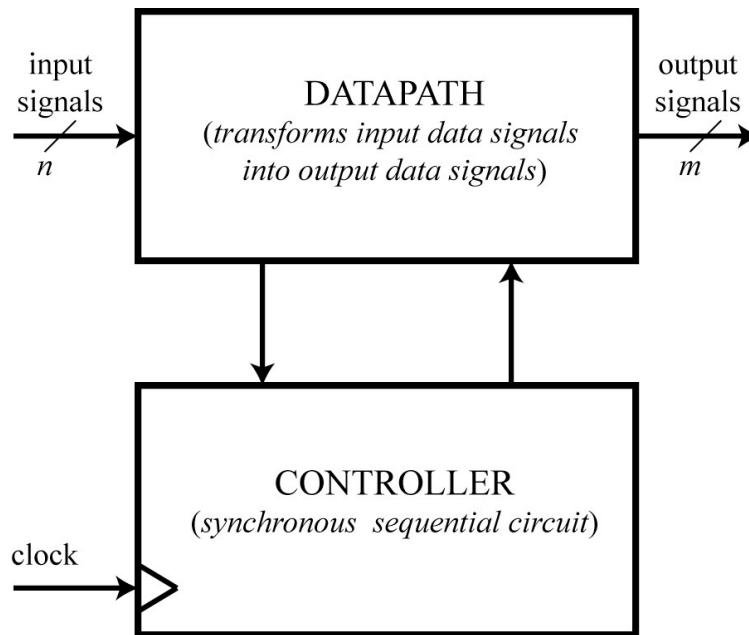

FSM Usage as Controller

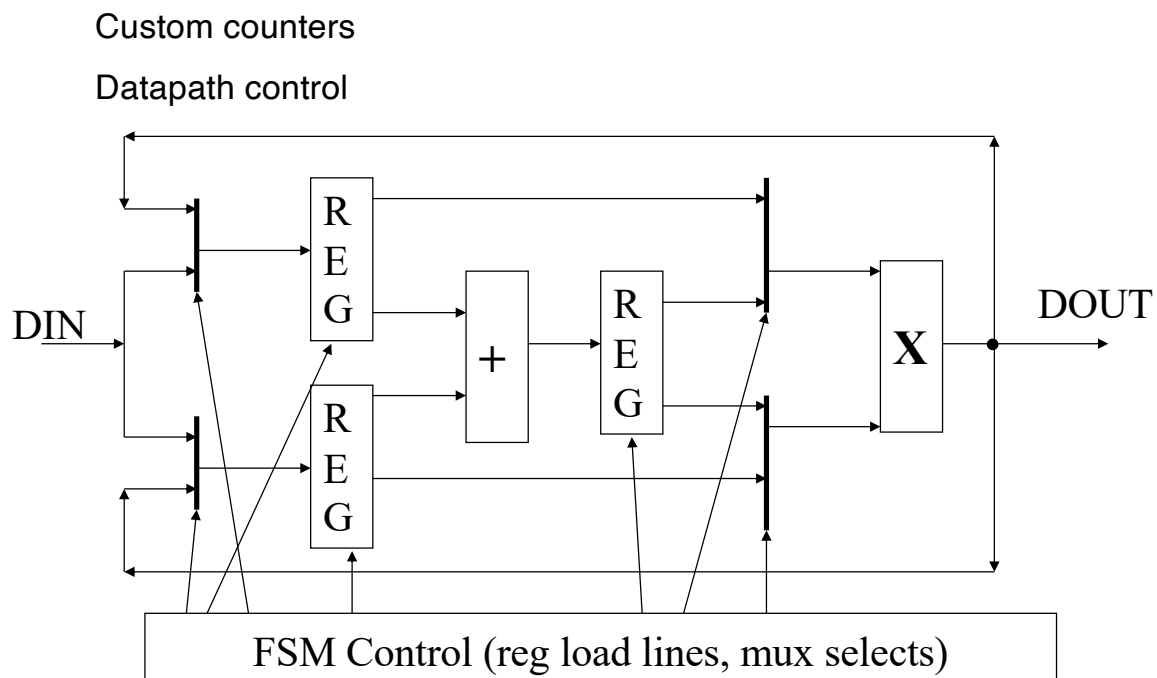

Summary

- We will be describing sequential systems via HDL.
- The HDL allows the synthesis of the design
- Will use common sequential building blocks extensively:
- Registers, Counters, Shift registers, Memories
- Basic storage element will be DFF